

# Su22-ENGR-40M-01 Prelab 4

Jannah Sabic El-Rayess

TOTAL POINTS

**37 / 37**

QUESTION 1

**1 P1 1 / 1**

✓ - **0 pts** Correct (amplitude 50mV, offset 1V)

- **0.25 pts** Incorrect P1 amplitude

- **0.25 pts** Incorrect P1 offset

- **1 pts** No Submission

- **3 pts** Late Submission

- **0.1 pts** didn't label amplitude

- **0.1 pts** Forgot units

- **0.5 pts** Calculations with no graph

- **0.2 pts** missing units

- **0.5 pts** Algebra mistake

- **1 pts** Incomplete

- **1.5 pts** Didn't use  $G = 5 + 80k/R_G$  eqn

- **2 pts** no work shown

QUESTION 2

**2 P2 2 / 2**

✓ - **0 pts** Correct (142-143)

- **0.3 pts** Used wrong voltage for Vout (should be +/- 1.5V) or Vin

- **1 pts** Used wrong formula

- **1 pts** Didn't calculate gain

- **0.5 pts** Used Vpp instead of 0.5Vpp

- **1 pts** didn't show work

- **1 pts** correct starting point

- **1.5 pts** Equations setup incorrectly

- **2 pts** no work

- **0.1 pts** Div by V instead of mV

- **1 pts** Incorrect

- **0.5 pts** Wrong Vref

- **0.2 pts** Didn't choose the correct Vin (i.e. chose wrong point to compare against the vout)

- **0 pts** Carry over error from P1

QUESTION 4

**4 P4 1 / 1**

✓ - **0 pts** Correct

- **0.2 pts** One incorrect pin

- **0.5 pts** Multiple incorrect pins

- **0.2 pts** missing Rg

- **0.25 pts** Forgot to label one of the two diagrams

- **1 pts** no work or over half the pins labelled incorrectly

- **0.1 pts** Missing/unlabeled pin

QUESTION 5

**5 P5 1 / 1**

✓ - **0 pts** Correct

- **0.2 pts** one incorrect pin (specified below)

- **0.25 pts** Forgot to label one of the two diagrams

- **0.5 pts** Multiple incorrectly labelled pins

- **1 pts** no work or over half the pins labelled incorrectly

- **0.1 pts** Missing/unlabeled pin

QUESTION 6

**6 P6 2 / 2**

✓ - **0 pts** Correct

- **0.1 pts** In terms of variables/non-numerical answer

- **1 pts** Not simplified

- **0.1 pts** missing j

- **0.1 pts** Sign error

- **0.3 pts** should be in standard form

- **1 pts** No work shown

QUESTION 3

**3 P3 2 / 2**

✓ - **0 pts** Correct (580 Ohm)

- **0 pts** carried error

- **0.1 pts** wrong units

- **1.5 pts** Incorrect work
- **2 pts** No submission
- **0.5 pts** Math error
- **0.2 pts** Error(s) #1
- **1 pts** Error(s) #2
- **0.2 pts** Missing 2pi
- **0.25 pts** Wrong capacitor value/units
- **1 pts** Incorrect; missing steps

#### QUESTION 7

#### 7 P7 1 / 1

- ✓ - **0 pts** Correct
- **0 pts** Carry over error
- **0.1 pts** Wrong sign on one current; gain should be negative
- **0.1 pts** Forgot j in frequency term
- **0.2 pts** Minor KCL error
- **1 pts** no work
- **0.5 pts** Want expression in terms of V\_out and V\_n

- **0.5 pts** incomplete
- **0.75 pts** Incorrect
- **0.2 pts** Math/Algebra error
- **0.1 pts** error(s) #1
- **0.2 pts** Zp expression not used in final answer.
- **0 pts** Carry over error from P6

#### QUESTION 8

#### 8 P8 2 / 2

- ✓ - **0 pts** Correct
- **0 pts** Carry over error
- **0.2 pts** sign error
- **0.2 pts** missing j
- **0.5 pts** incorrect band pass gain
- **0.5 pts** incorrect corner frequency
- **0.5 pts** algebra mistake
- **1 pts** no work
- **0.3 pts** should be in standard form
- **0.5 pts** Error(s)
- **2 pts** No submission
- **0.1 pts** Minor Error
- **1.5 pts** Incorrect

#### QUESTION 9

#### 9 P9 2 / 2

- ✓ - **0 pts** Correct (20dB at low frequencies, -\\$infty\\$ at high frequencies)
- **0.1 pts** gave high frequency gain in linear gain (not dB)
- **0.5 pts** Forgot to convert to dB
- **0.5 pts** incorrect at low frequencies
- **0.5 pts** incorrect at high frequencies
- **2 pts** missing
- **0.1 pts** gave low frequency gain in linear gain (not dB)
- **0 pts** Error carried over from previous part
- **1 pts** Incorrect
- **1.5 pts** Incorrect
- **2 pts** No submission
- **0.2 pts** Error(s) #1

#### QUESTION 10

#### 10 P10 3 / 3

- ✓ - **0 pts** Correct
- **0.1 pts** Near correct/ambiguous fall-off slope
- **0.3 pts** Incorrect corner frequency
- **0.5 pts** did not label important feature corner frequency
- **0.3 pts** Corner frequency in wrong place on graph
- **0.5 pts** Incorrect low frequency gain
- **0.5 pts** incorrect fall-off slope (should be 20db/decade)
- **0.5 pts** fall-off slope ambiguous or not specified
- **0.5 pts** Corner frequency not given or labeled
- **1 pts** Incorrect/Missing Corner Frequency
- **1.5 pts** not shaped like a low pass filter
- **3 pts** no work
- **0.5 pts** Error(s)
- **0.3 pts** Error(s)
- **3 pts** Problem blank

#### QUESTION 11

#### 11 P11 1 / 1

- ✓ - **0 pts** Correct (lowpass)
- **0.5 pts** incorrect

- 1 pts no work
- 1 pts Problem blank

QUESTION 12

12 P12 3 / 3

✓ - 0 pts Correct

- 0.2 pts Sign error
- 0.2 pts missing j
- 0.5 pts algebra error
- 0.5 pts Correct but not simplified
- 1 pts incorrect pass band gain
- 1 pts incorrect cutoff frequency
- 1.5 pts Not simplified or no/little work given
- 1.5 pts no work
- 0.2 pts Error(s) #1
- 0.3 pts Not in standard form
- 1 pts Incorrect
- 1.5 pts Incorrect
- 3 pts Problem blank

QUESTION 13

13 P13 2 / 2

✓ - 0 pts Correct (-\$ $\infty$  at low frequencies and 20dB at high frequencies)

- 0.1 pts Said +infinity at low frequencies
- 0.1 pts gave linear gain at low frequencies
- 0.5 pts Forgot to convert to dB
- 0.5 pts incorrect dB conversion
- 0.5 pts incorrect at low frequencies
- 0.5 pts incorrectly said approaches 0dB at high frequencies
- 0.5 pts incorrect at high frequencies
- 0.5 pts Incorrect work or derivation
- 1 pts Incorrect
- 1.5 pts Incorrect
- 0.2 pts Small error
- 2 pts no work
- 2 pts Problem blank

QUESTION 14

14 P14 3 / 3

✓ - 0 pts Correct (corner frequency .3, high pass

20dB)

- 0.1 pts minor error
- 0.3 pts slope mislabeled
- 0.3 pts Corner frequency unlabeled
- 0.5 pts slope at low frequencies not specified or ambiguous
- 0.5 pts Ambiguous corner frequency
- 0.5 pts incorrect high frequency gain
- 0.5 pts slope at low frequencies should be 20dB/decade
- 1 pts Wrong corner frequency
- 1 pts line should be flat at high frequencies
- 1.5 pts Ambiguous/unlabeled graph with generally correct shape
- 2 pts drew lowpass filter
- 0 pts Carry over error from P12 or P13
- 3 pts no work
- 3 pts Problem blank / Major error
- 0.1 pts Wrong corner frequency on graph

QUESTION 15

15 P15 1 / 1

- ✓ - 0 pts Correct (high pass)
- 0.5 pts incorrect
  - 1 pts no work

QUESTION 16

16 P16 1 / 1

- ✓ - 0 pts Correct
- 0.1 pts sign error
  - 0.2 pts Error(s) #1
  - 0.25 pts One incorrect current equation
  - 0.5 pts should be a nodal equation
  - 0.5 pts answer not simplified
  - 1 pts no work
  - 1 pts Incorrect
  - 1 pts problem blank
  - 0.2 pts Nodal equation set up incorrectly

QUESTION 17

17 P17 3 / 3

✓ - 0 pts Correct

- **0 pts** Carry over error
- **0.2 pts** incorrect sign
- **0.2 pts** missing j
- **0.5 pts** algebra error
- **1.5 pts** denominator should have higher order f terms
- **2 pts** wrong approach
- **3 pts** No submission
- **0.75 pts** Right approach but no numerical values given/not simplified to std form
- **0.2 pts** One incorrect fc
- **1.5 pts** No work
- **0.3 pts** Not in standard form
- **0.3 pts** Answer not simplified
- **0.1 pts** missing fc1
- **3 pts** problem blank
- **0.3 pts** Low corner frequency incorrectly graphed
- **0.3 pts** High corner frequency incorrectly graphed
- **0.5 pts** one incorrect corner frequency
- **0.5 pts** graphing errors (see comments or graph)
- **0.5 pts** Incorrect bandpass gain
- **1 pts** Incorrect corner frequencies
- **0.5 pts** slope incorrect (should be 20db/decade)
- **0.5 pts** Corner frequencies not labeled
- **1 pts** forgot to label corner frequencies
- **2 pts** Not shaped like a bandpass filter
- **1 pts** Incorrect low/high frequency behavior
- **3 pts** Incomplete
- **0 pts** Carry over error from P18, but graph is correct.
- **1.5 pts** Graph vague, corner frequencies not labeled but correct shape

#### QUESTION 18

##### 18 P18 2 / 2

- ✓ - **0 pts** Correct (should approach  $-\infty$  for high and low frequencies, passband should have gain of 20dB)
- **0.5 pts** no answer for bandpass gain
  - **0.5 pts** Incorrect bandpass gain (accept anything between 10-20dB)
  - **0.5 pts** infinity instead of -infinity
  - **0.5 pts** Incorrectly said zero for low/high frequency
  - **0.5 pts** incorrect low frequencies
  - **0.5 pts** incorrect high frequencies
  - **2 pts** no work
  - **0.5 pts** Did not convert to dB
  - **2 pts** problem blank
  - **0.4 pts** No answer for high/low frequency case.
  - **1 pts** no numerical value given for multiple regions

#### QUESTION 19

##### 19 P19 3 / 3

- ✓ - **0 pts** Correct (bandpass 20dB, corner frequencies at .33 and 15.9 Hz)
- **0.3 pts** said slope is +/- 1 for low and high frequency regions

#### QUESTION 20

##### 20 P20 1 / 1

- ✓ - **0 pts** Correct (Bandpass)
- **0.5 pts** Incorrect
  - **1 pts** no submission




- P1:** Consider the circuit on the right. We use a test input signal, representing a "heartbeat", of a 1 mVpp sine wave with a 10 mV offset. The test input signal ( $V_{in}^+ - V_{in}^-$ ) is graphed below right.

We connect  $V_+$  and  $V_-$  to 5 V and ground respectively, and we set  $G = 100$ .

Sketch the output waveform. Label the offset, minimum and maximum voltages.

*Hint: Equation (1) on page 2 might be helpful.*

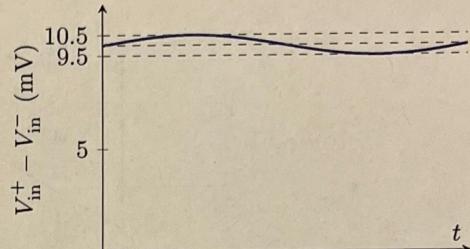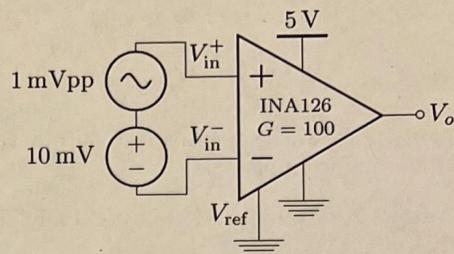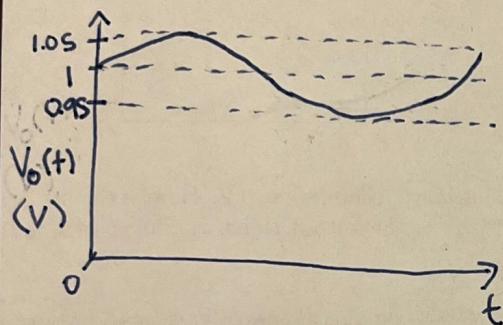*Hint: The gain applies to the entire input signal, including the offset!*



$$\begin{aligned} \text{offset } &t = 1\text{V} \\ \text{max} &= 1.05\text{V} \\ \text{min} &= 0.95\text{V} \end{aligned}$$

In practice, clipping actually occurs *before* the output voltage would hit the rails.

- P2:** To be safe, we will try to keep our peak output voltages 1 V away from our supplies ( $-1.5\text{V} < V_{out} < 1.5\text{V}$ ). With an input signal of amplitude of 1 mVpp but with offsets of up to  $\pm 10\text{mV}$ , use equation (1) to calculate the maximum gain you can achieve with your instrumentation amplifier, before you risk clipping.

$$V_o = G(\text{signal}) + V_{ref}$$

$$1.5\text{V} = G(10.5\text{mV})$$

$$G = 143$$

To set  $G$ , we choose a suitable resistor  $R_G$ . The INA126 datasheet indicates how to choose  $R_G$ .

- P3:** The datasheet gives an equation that describes what the gain  $G$  is, in terms of the resistor  $R_G$ . Using the INA126 datasheet on Canvas, find this equation, and use it to calculate a resistor value  $R_G$  that will give you the gain you calculated in question P2.

$$G = 5 + \frac{80k\Omega}{R_G}$$

$$143 = 5 + \frac{80k\Omega}{R_G}$$

$$R_G = 580\Omega$$

1 P1 1/1

✓ - **0 pts** Correct (amplitude 50mV, offset 1V)

- **0.25 pts** Incorrect P1 amplitude

- **0.25 pts** Incorrect P1 offset

- **1 pts** No Submission

- **3 pts** Late Submission

- **0.1 pts** didn't label amplitude

- **0.1 pts** Forgot units

- **0.5 pts** Calculations with no graph




- P1:** Consider the circuit on the right. We use a test input signal, representing a "heartbeat", of a 1 mVpp sine wave with a 10 mV offset. The test input signal ( $V_{in}^+ - V_{in}^-$ ) is graphed below right.

We connect  $V_+$  and  $V_-$  to 5 V and ground respectively, and we set  $G = 100$ .

Sketch the output waveform. Label the offset, minimum and maximum voltages.

*Hint: Equation (1) on page 2 might be helpful.*

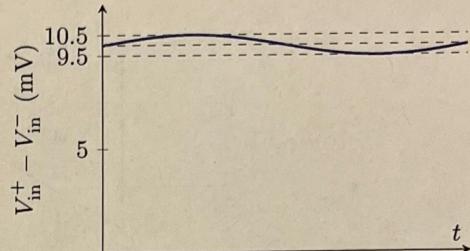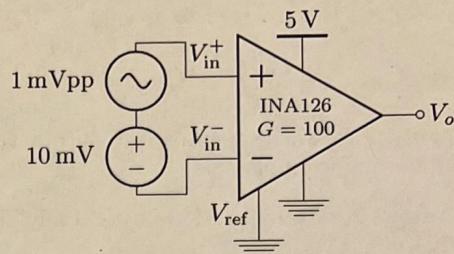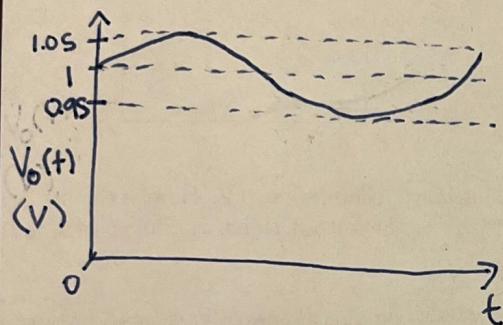*Hint: The gain applies to the entire input signal, including the offset!*



$$\begin{aligned} \text{offset } &t = 1\text{V} \\ \text{max} &= 1.05\text{V} \\ \text{min} &= 0.95\text{V} \end{aligned}$$

In practice, clipping actually occurs *before* the output voltage would hit the rails.

- P2:** To be safe, we will try to keep our peak output voltages 1 V away from our supplies ( $-1.5\text{V} < V_{out} < 1.5\text{V}$ ). With an input signal of amplitude of 1 mVpp but with offsets of up to  $\pm 10\text{mV}$ , use equation (1) to calculate the maximum gain you can achieve with your instrumentation amplifier, before you risk clipping.

$$V_o = G(\text{signal}) + V_{ref}$$

$$1.5\text{V} = G(10.5\text{mV})$$

$$G = 143$$

To set  $G$ , we choose a suitable resistor  $R_G$ . The INA126 datasheet indicates how to choose  $R_G$ .

- P3:** The datasheet gives an equation that describes what the gain  $G$  is, in terms of the resistor  $R_G$ . Using the INA126 datasheet on Canvas, find this equation, and use it to calculate a resistor value  $R_G$  that will give you the gain you calculated in question P2.

$$G = 5 + \frac{80k\Omega}{R_G}$$

$$143 = 5 + \frac{80k\Omega}{R_G}$$

$$R_G = 580\Omega$$

## 2 P2 2 / 2

### ✓ - 0 pts Correct (142-143)

- 0.3 pts Used wrong voltage for Vout (should be +/- 1.5V) or Vin
- 1 pts Used wrong formula
- 1 pts Didn't calculate gain
- 0.5 pts Used Vpp instead of 0.5Vpp
- 1 pts didn't show work
- 1 pts correct starting point
- 1.5 pts Equations setup incorrectly
- 2 pts no work
- 0.1 pts Div by V instead of mV
- 1 pts Incorrect
- 0.5 pts Wrong Vref
- 0.2 pts Didn't choose the correct Vin (i.e. chose wrong point to compare against the vout)
- 0 pts Carry over error from P1




- P1:** Consider the circuit on the right. We use a test input signal, representing a "heartbeat", of a 1 mVpp sine wave with a 10 mV offset. The test input signal ( $V_{in}^+ - V_{in}^-$ ) is graphed below right.

We connect  $V_+$  and  $V_-$  to 5 V and ground respectively, and we set  $G = 100$ .

Sketch the output waveform. Label the offset, minimum and maximum voltages.

*Hint: Equation (1) on page 2 might be helpful.*

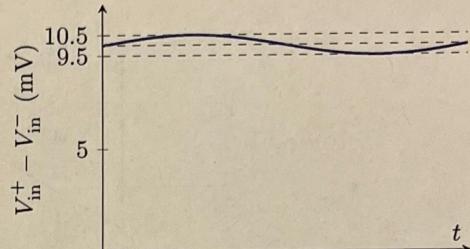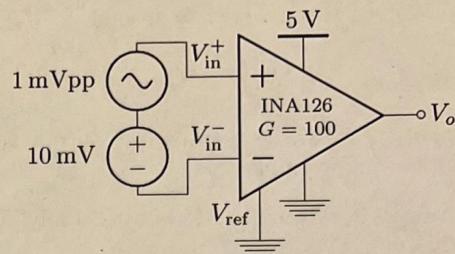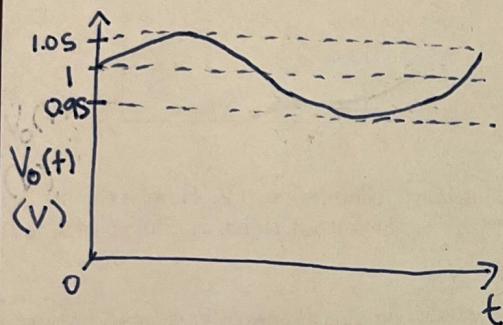*Hint: The gain applies to the entire input signal, including the offset!*



$$\begin{aligned} \text{offset } &t = 1\text{V} \\ \text{max} &= 1.05\text{V} \\ \text{min} &= 0.95\text{V} \end{aligned}$$

In practice, clipping actually occurs *before* the output voltage would hit the rails.

- P2:** To be safe, we will try to keep our peak output voltages 1 V away from our supplies ( $-1.5\text{V} < V_{out} < 1.5\text{V}$ ). With an input signal of amplitude of 1 mVpp but with offsets of up to  $\pm 10\text{mV}$ , use equation (1) to calculate the maximum gain you can achieve with your instrumentation amplifier, before you risk clipping.

$$V_o = G(\text{signal}) + V_{ref}$$

$$1.5\text{V} = G(10.5\text{mV})$$

$$G = 143$$

To set  $G$ , we choose a suitable resistor  $R_G$ . The INA126 datasheet indicates how to choose  $R_G$ .

- P3:** The datasheet gives an equation that describes what the gain  $G$  is, in terms of the resistor  $R_G$ . Using the INA126 datasheet on Canvas, find this equation, and use it to calculate a resistor value  $R_G$  that will give you the gain you calculated in question P2.

$$G = 5 + \frac{80k\Omega}{R_G}$$

$$143 = 5 + \frac{80k\Omega}{R_G}$$

$$R_G = 580\Omega$$

3 P3 2 / 2

✓ - **0 pts** Correct (580 Ohm)

- **0 pts** carried error

- **0.1 pts** wrong units

- **0.2 pts** missing units

- **0.5 pts** Algebra mistake

- **1 pts** Incomplete

- **1.5 pts** Didn't use  $G = 5 + 80k/R_G$  eqn

- **2 pts** no work shown


*Hint: The equation appears three times on page 1 of the datasheet.*

One last thing on the instrumentation amplifier: The INA126 comes in a “dual inline” package with eight pins (DIP-8). We’ll need to know which pin corresponds to which terminal.


- P4:** Using the INA126 datasheet on Canvas, label each of the eight terminals on the schematic symbol with their corresponding pin numbers, and each of the eight pins on the package diagram with their corresponding terminal names.

*Remark:  $V_{in}^+$  and  $V_{in}^-$  are the input terminals.  $V_+$  and  $V_-$  are the power supply terminals.*

*Label pin numbers on schematic symbol:*

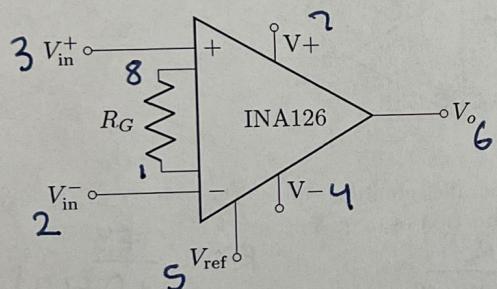

*Label pin names on package diagram:*

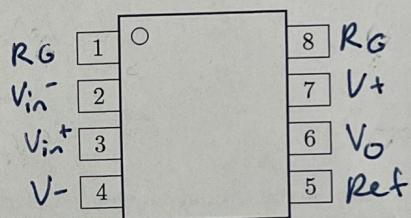

### 3.2 Operational Amplifier (MCP601)

We'll use an op-amp to implement the bandpass filter stage of our circuit. While we're looking at datasheets, let's start by taking note of its pinout. The MCP601 also comes in a DIP-8 package.

- P5:** Using the MCP601 datasheet on Canvas, label each of the eight terminals on the schematic symbol with their corresponding pin numbers, and each of the eight pins on the package diagram with their corresponding terminal names.


*Remark:  $V_{in}^+$  and  $V_{in}^-$  are the input terminals. This manufacturer calls the positive power supply terminal  $V_{DD}$ , and the negative power supply terminal  $V_{SS}$ . “NC” stands for “not connected”.*

4 P4 1 / 1


✓ - **0 pts** Correct

- **0.2 pts** One incorrect pin
- **0.5 pts** Multiple incorrect pins
- **0.2 pts** missing Rg
- **0.25 pts** Forgot to label one of the two diagrams
- **1 pts** no work or over half the pins labelled incorrectly
- **0.1 pts** Missing/unlabeled pin


Label pin numbers on schematic symbol:

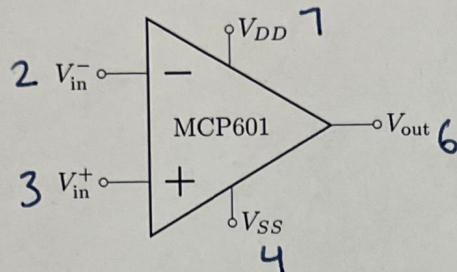

Label pin names on package diagram:

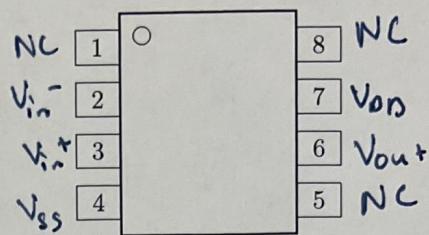

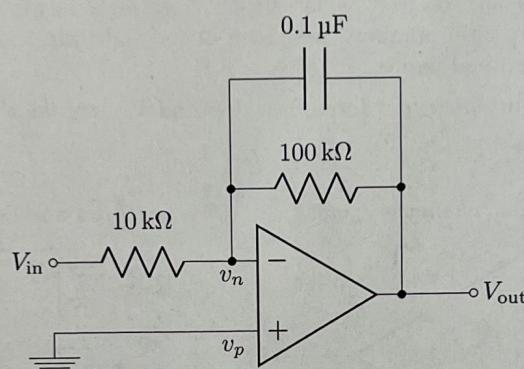For questions P6 through P11, consider the circuit below. In all circuits in this lab,  $V_{DD} = 2.5\text{ V}$  and  $V_{ss} = -2.5\text{ V}$ .



P6: What is the overall impedance of the parallel combination of the  $100\text{ k}\Omega$  resistor and  $0.1\text{ }\mu\text{F}$  capacitor in this circuit? This will be a function of frequency.

$$\frac{1}{R_T} = \frac{1}{R} + 2\pi f j C \quad R_T = \frac{R}{1 + 2R\pi f j C}$$


$$R_T = \frac{1}{\frac{1}{R} + 2\pi f j C}$$

$$R_T = \frac{1ES}{1 + 2(1ES)\pi f j (1E-7)}$$

$$R_T = \frac{1ES}{1 + 0.02\pi f j}$$

$$R_T = \frac{100k\Omega}{1 + 20\pi msfj}$$

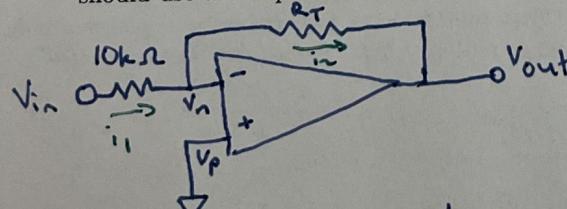P7: Use Kirchoff's current law, applied at the node at the inverting (-) input to the op-amp,  $v_n$ , to find a relationship between  $V_{in}$ ,  $V_{out}$  and  $v_n$ . You can assume that the op-amp is ideal, and you should use the impedance result from question P6.



$$i_1 = i_2$$

$$\frac{V_{in}}{R} = i$$

$$\frac{V_{in}}{10k\Omega} = -\frac{V_{out}}{R_T}$$

$$-V_{out}/10k\Omega = V_{in}/R_T$$

$$-\frac{V_{out}}{V_{in}} = \frac{R_T}{10k\Omega}$$

$$-\frac{V_{out}}{V_{in}} = \frac{100k\Omega}{1 + 20\pi msfj} \cdot \frac{1}{10k\Omega}$$

$$-\frac{V_{out}}{V_{in}} = \frac{10}{1 + 20\pi msfj}$$

$$V_{out} = -V_{in} \left( \frac{10}{1 + 20\pi msfj} \right)$$


$$V_n = 0V$$

5 P5 1/1


✓ - **0 pts** Correct

- **0.2 pts** one incorrect pin (specified below)
- **0.25 pts** Forgot to label one of the two diagrams
- **0.5 pts** Multiple incorrectly labelled pins
- **1 pts** no work or over half the pins labelled incorrectly
- **0.1 pts** Missing/unlabeled pin


Label pin numbers on schematic symbol:

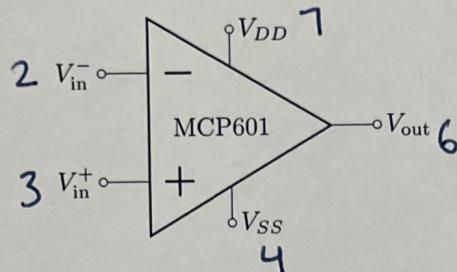

Label pin names on package diagram:

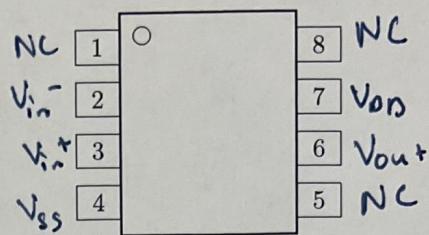

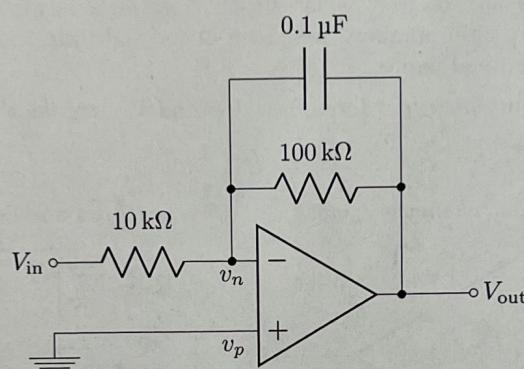For questions P6 through P11, consider the circuit below. In all circuits in this lab,  $V_{DD} = 2.5\text{ V}$  and  $V_{ss} = -2.5\text{ V}$ .



P6: What is the overall impedance of the parallel combination of the  $100\text{ k}\Omega$  resistor and  $0.1\text{ }\mu\text{F}$  capacitor in this circuit? This will be a function of frequency.

$$\frac{1}{R_T} = \frac{1}{R} + 2\pi f j C \quad R_T = \frac{R}{1 + 2R\pi f j C}$$


$$R_T = \frac{1}{\frac{1}{R} + 2\pi f j C}$$

$$R_T = \frac{1ES}{1 + 2(1ES)\pi f j (1E-7)}$$

$$R_T = \frac{1ES}{1 + 0.02\pi f j}$$

$$R_T = \frac{100k\Omega}{1 + 20\pi msfj}$$

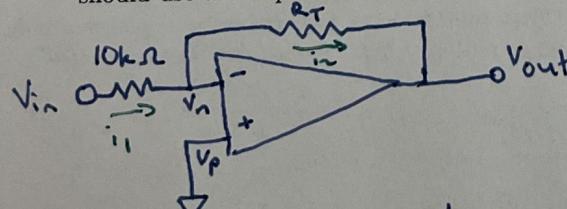P7: Use Kirchoff's current law, applied at the node at the inverting (-) input to the op-amp,  $v_n$ , to find a relationship between  $V_{in}$ ,  $V_{out}$  and  $v_n$ . You can assume that the op-amp is ideal, and you should use the impedance result from question P6.



$$-\frac{V_{out}}{V_{in}} = \frac{100k\Omega}{1 + 20\pi msfj} \cdot \frac{1}{10k\Omega}$$

$$i_1 = i_2$$

$$\frac{V_{in}}{R} = i$$

$$\frac{V_{in}}{10k\Omega} = -\frac{V_{out}}{R_T}$$

$$-V_{out}/10k\Omega = V_{in}/R_T$$

$$-\frac{V_{out}}{V_{in}} = \frac{R_T}{10k\Omega}$$

$$-\frac{V_{out}}{V_{in}} = \frac{10}{1 + 20\pi msfj}$$

$$V_{out} = -V_{in} \left( \frac{10}{1 + 20\pi msfj} \right)$$


$$V_n = 0V$$

## 6 P6 2 / 2


✓ - **0 pts** Correct

- **0.1 pts** In terms of variables/non-numerical answer
- **1 pts** Not simplified
- **0.1 pts** missing j
- **0.1 pts** Sign error
- **0.3 pts** should be in standard form
- **1 pts** No work shown
- **1.5 pts** Incorrect work
- **2 pts** No submission
- **0.5 pts** Math error
- **0.2 pts** Error(s) #1
- **1 pts** Error(s) #2
- **0.2 pts** Missing 2pi
- **0.25 pts** Wrong capacitor value/units
- **1 pts** Incorrect; missing steps


Label pin numbers on schematic symbol:

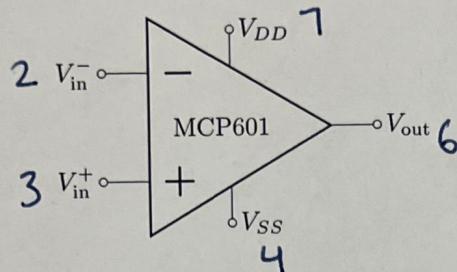

Label pin names on package diagram:

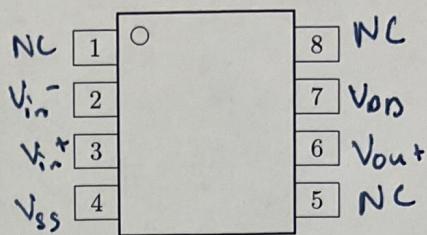

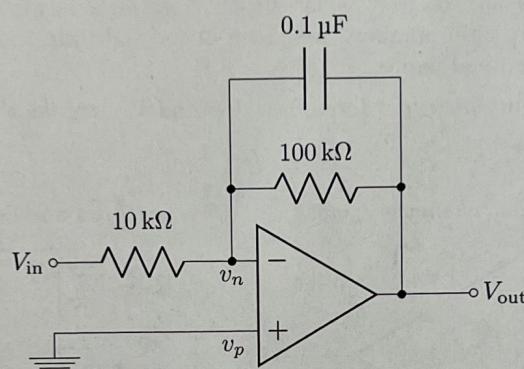For questions P6 through P11, consider the circuit below. In all circuits in this lab,  $V_{DD} = 2.5\text{ V}$  and  $V_{ss} = -2.5\text{ V}$ .



P6: What is the overall impedance of the parallel combination of the  $100\text{ k}\Omega$  resistor and  $0.1\text{ }\mu\text{F}$  capacitor in this circuit? This will be a function of frequency.

$$\frac{1}{R_T} = \frac{1}{R} + 2\pi f j C \quad R_T = \frac{R}{1 + 2R\pi f j C}$$


$$R_T = \frac{1}{\frac{1}{R} + 2\pi f j C}$$

$$R_T = \frac{1ES}{1 + 2(1ES)\pi f j (1E-7)}$$

$$R_T = \frac{1ES}{1 + 0.02\pi f j}$$

$$R_T = \frac{100k\Omega}{1 + 20\pi msfj}$$

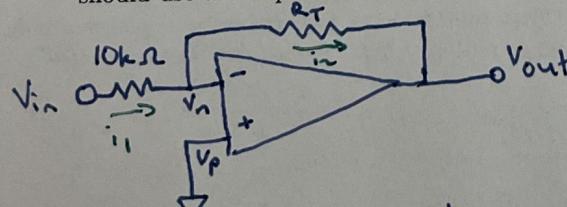P7: Use Kirchoff's current law, applied at the node at the inverting (-) input to the op-amp,  $v_n$ , to find a relationship between  $V_{in}$ ,  $V_{out}$  and  $v_n$ . You can assume that the op-amp is ideal, and you should use the impedance result from question P6.



$$i_1 = i_2$$

$$\frac{V_{in}}{R} = i$$

$$\frac{V_{in}}{10k\Omega} = \frac{-V_{out}}{R_T}$$

$$-V_{out}/10k\Omega = V_{in}/R_T$$

$$\frac{-V_{out}}{V_{in}} = \frac{R_T}{10k\Omega}$$

$$\frac{-V_{out}}{V_{in}} = \frac{100k\Omega}{1 + 20\pi msfj} \cdot \frac{1}{10k\Omega}$$

$$\frac{-V_{out}}{V_{in}} = \frac{10}{1 + 20\pi msfj}$$

$$V_{out} = -V_{in} \left( \frac{10}{1 + 20\pi msfj} \right)$$

$$V_n = 0V$$

7 P7 1 / 1

✓ - 0 pts Correct

- 0 pts Carry over error

- 0.1 pts Wrong sign on one current; gain should be negative

- 0.1 pts Forgot j in frequency term

- 0.2 pts Minor KCL error

- 1 pts no work

- 0.5 pts Want expression in terms of V\_out and V\_n

- 0.5 pts incomplete

- 0.75 pts Incorrect

- 0.2 pts Math/Algebra error

- 0.1 pts error(s) #1

- 0.2 pts Zp expression not used in final answer.

- 0 pts Carry over error from P6

P8: Using your equation from P7, find an expression for the transfer function for this circuit as a function of frequency, which should be in the form  $\frac{V_{out}}{V_{in}} = \frac{A}{1+j\frac{f}{f_c}}$ .

$$V_{out} = -V_{in} \left( \frac{10}{1+20\pi ms f j} \right)$$

$$\frac{V_{out}}{V_{in}} = -\frac{10}{1+20\pi ms f j}$$

$$1 = 20\pi ms f$$

$$f = 15.9$$

$$\boxed{\frac{V_{out}}{V_{in}} = -\frac{10}{1+j\frac{f}{15.9}}}$$

P9: What is the magnitude of this transfer function, in dB, (i) at very low frequencies? (ii) at very high frequencies? (Remember, the magnitude in dB is given by  $20 \log_{10} \left| \frac{V_{out}}{V_{in}} \right|$ .)

$$\lim_{f \rightarrow 0} -\frac{10}{1+j\frac{f}{15.9}} = -\frac{10}{1} = -10$$

$$\lim_{f \rightarrow \infty} -\frac{10}{1+j\frac{f}{15.9}} = 0$$

$$20 \log | -10 | = 20$$

$$\lim_{n \rightarrow 0} 20 \log | n | = -\infty$$

$$\boxed{\begin{aligned} & (i) 20 \\ & (ii) -\infty \end{aligned}}$$

8 P8 2 / 2

✓ - 0 pts Correct

- 0 pts Carry over error
- 0.2 pts sign error
- 0.2 pts missing j
- 0.5 pts incorrect band pass gain
- 0.5 pts incorrect corner frequency
- 0.5 pts algebra mistake
- 1 pts no work
- 0.3 pts should be in standard form
- 0.5 pts Error(s)
- 2 pts No submission
- 0.1 pts Minor Error
- 1.5 pts Incorrect

P8: Using your equation from P7, find an expression for the transfer function for this circuit as a function of frequency, which should be in the form  $\frac{V_{out}}{V_{in}} = \frac{A}{1+j\frac{f}{f_c}}$ .

$$V_{out} = -V_{in} \left( \frac{10}{1+20\pi ms f j} \right)$$

$$\frac{V_{out}}{V_{in}} = -\frac{10}{1+20\pi ms f j}$$

$$1 = 20\pi ms f$$

$$f = 15.9$$

$$\boxed{\frac{V_{out}}{V_{in}} = -\frac{10}{1+j\frac{f}{15.9}}}$$

P9: What is the magnitude of this transfer function, in dB, (i) at very low frequencies? (ii) at very high frequencies? (Remember, the magnitude in dB is given by  $20 \log_{10} \left| \frac{V_{out}}{V_{in}} \right|$ .)

$$\lim_{f \rightarrow 0} -\frac{10}{1+j\frac{f}{15.9}} = -\frac{10}{1} = -10$$

$$\lim_{f \rightarrow \infty} -\frac{10}{1+j\frac{f}{15.9}} = 0$$

$$20 \log | -10 | = 20$$

$$\lim_{n \rightarrow 0} 20 \log | n | = -\infty$$

$$\boxed{\begin{aligned} \text{(i)} & 20 \\ \text{(ii)} & -\infty \end{aligned}}$$

9 P9 2 / 2

✓ - **0 pts** Correct (20dB at low frequencies,  $-\infty$  at high frequencies)

- **0.1 pts** gave high frequency gain in linear gain (not dB)

- **0.5 pts** Forgot to convert to dB

- **0.5 pts** incorrect at low frequencies

- **0.5 pts** incorrect at high frequencies

- **2 pts** missing

- **0.1 pts** gave low frequency gain in linear gain (not dB)

- **0 pts** Error carried over from previous part


- **1 pts** Incorrect

- **1.5 pts** Incorrect

- **2 pts** No submission

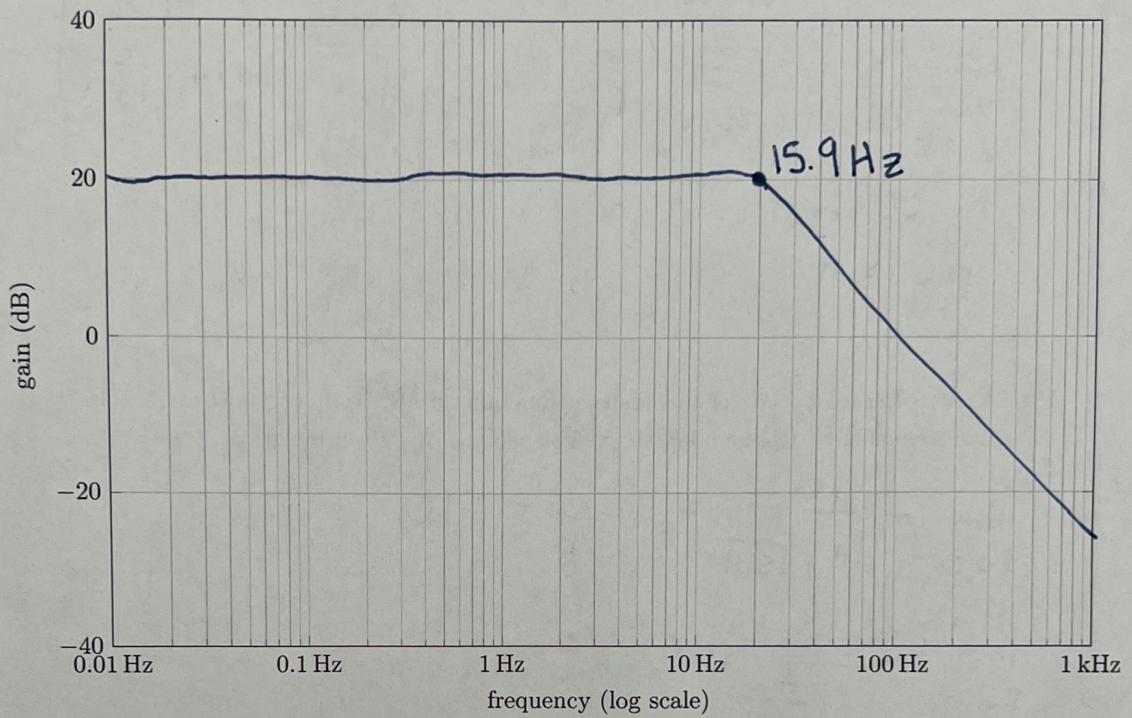- **0.2 pts** Error(s) #1

P10: On the axes below, draw the Bode magnitude plot for this circuit. Label all important features of the plot.



P11: Using your Bode magnitude plot, is this a lowpass, highpass, bandpass or bandstop filter?


Lowpass filter

10 P10 3 / 3

✓ - 0 pts Correct

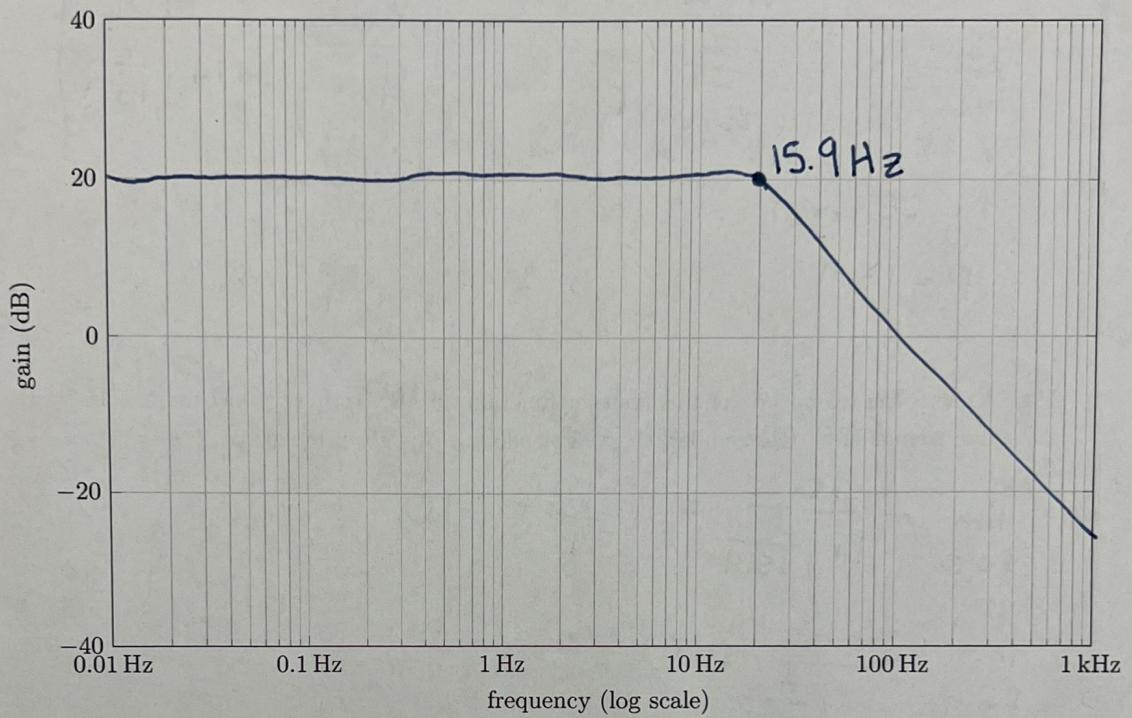- 0.1 pts Near correct/ambiguous fall-off slope
- 0.3 pts Incorrect corner frequency
- 0.5 pts did not label important feature corner frequency
- 0.3 pts Corner frequency in wrong place on graph
- 0.5 pts Incorrect low frequency gain
- 0.5 pts incorrect fall-off slope (should be 20db/decade)
- 0.5 pts fall-off slope ambiguous or not specified
- 0.5 pts Corner frequency not given or labeled
- 1 pts Incorrect/Missing Corner Frequency
- 1.5 pts not shaped like a low pass filter
- 3 pts no work
- 0.5 pts Error(s)
- 0.3 pts Error(s)
- 3 pts Problem blank

P10: On the axes below, draw the Bode magnitude plot for this circuit. Label all important features of the plot.



P11: Using your Bode magnitude plot, is this a lowpass, highpass, bandpass or bandstop filter?

Lowpass filter

11 P11 1 / 1


✓ - 0 pts Correct (lowpass)

- 0.5 pts incorrect

- 1 pts no work

- 1 pts Problem blank

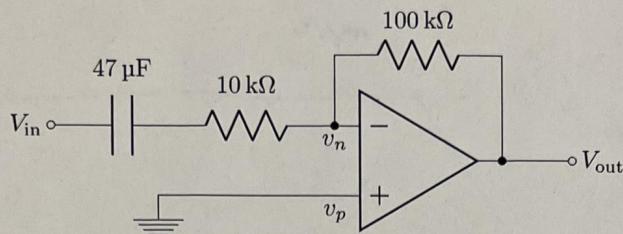For questions P12 through P15, consider the following circuit.



**P12:** Using the same steps as for the previous circuit, find an equation for the transfer function of this circuit.

*Hint: This transfer function will be in the form  $\frac{j\frac{f}{f_{c1}}}{1+j\frac{f}{f_{c2}}}$ .*

$$R_T = \frac{1}{2\pi f j c} + R$$

$$R_T = \frac{1}{2\pi f j c} + \frac{R 2\pi f j c}{2\pi f j c}$$

$$R_T = \frac{1 + 2\pi R f j c}{2\pi f j c}$$

$$\frac{V_{out}}{V_{in}} = - \frac{100 k\Omega}{1 + 2\pi R f j c}$$

$$\frac{V_{out}}{V_{in}} = -100 k\Omega \cdot \frac{2\pi f j 47 E - 6}{1 + 2\pi 10 k\Omega f j 47 E - 6}$$

$$\frac{V_{out}}{V_{in}} = \frac{-9.4 \pi s f j}{1 + 0.94 \pi s f j}$$

$$f_{c2} = \frac{1}{0.94 \pi} = 0.339$$

$$f_{c1} = \frac{1}{9.4 \pi} = 0.0339$$

$$\boxed{\frac{V_{out}}{V_{in}} = -j \frac{f}{0.0339}}$$

**P13:** What is the magnitude of this transfer function, in dB, (i) at very low frequencies? (ii) at very high frequencies? (Remember, the magnitude in dB is given by  $20 \log_{10} \left| \frac{V_{out}}{V_{in}} \right|$ .)

$$\lim_{f \rightarrow 0} \frac{V_{out}}{V_{in}} = 0 \quad \lim_{n \rightarrow 0} 20 \log_{10} 1 = -\infty$$

(i)  $-\infty$

$$\lim_{f \rightarrow \infty} \frac{V_{out}}{V_{in}} = -10 \quad 20 \log_{10} 1 - 10 = 20$$

(ii) 20

**P14:** On the axes below, draw the Bode magnitude plot for this circuit. Label all important features of the plot.

12 P12 3 / 3

✓ - 0 pts Correct

- 0.2 pts Sign error

- 0.2 pts missing j

- 0.5 pts algebra error

- 0.5 pts Correct but not simplified

- 1 pts incorrect pass band gain

- 1 pts incorrect cutoff frequency

- 1.5 pts Not simplified or no/little work given

- 1.5 pts no work

- 0.2 pts Error(s) #1


- 0.3 pts Not in standard form

- 1 pts Incorrect

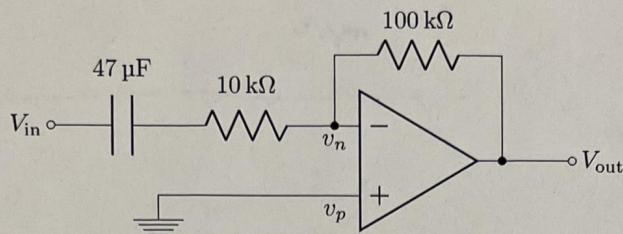- 1.5 pts Incorrect

- 3 pts Problem blank

For questions P12 through P15, consider the following circuit.



**P12:** Using the same steps as for the previous circuit, find an equation for the transfer function of this circuit.

*Hint: This transfer function will be in the form  $\frac{j\frac{f}{f_{c1}}}{1+j\frac{f}{f_{c2}}}$ .*

$$R_T = \frac{1}{2\pi f j c} + R$$

$$R_T = \frac{1}{2\pi f j c} + \frac{R 2\pi f j c}{2\pi f j c}$$

$$R_T = \frac{1 + 2\pi R f j c}{2\pi f j c}$$

$$\frac{V_{out}}{V_{in}} = - \frac{100 k\Omega}{1 + 2\pi R f j c}$$

$$\frac{V_{out}}{V_{in}} = -100 k\Omega \cdot \frac{2\pi f j 47 E - 6}{1 + 2\pi 10 k\Omega f j 47 E - 6}$$

$$\frac{V_{out}}{V_{in}} = \frac{-9.4 \pi s f j}{1 + 0.94 \pi s f j}$$

$$f_{c2} = \frac{1}{0.94 \pi} = 0.339$$

$$f_{c1} = \frac{1}{9.4 \pi} = 0.0339$$

$$\boxed{\frac{V_{out}}{V_{in}} = -j \frac{f}{0.0339}}$$

**P13:** What is the magnitude of this transfer function, in dB, (i) at very low frequencies? (ii) at very high frequencies? (Remember, the magnitude in dB is given by  $20 \log_{10} \left| \frac{V_{out}}{V_{in}} \right|$ .)

$$\lim_{f \rightarrow 0} \frac{V_{out}}{V_{in}} = 0 \quad \lim_{n \rightarrow 0} 20 \log_{10} 1 = -\infty$$

(i)  $-\infty$

$$\lim_{f \rightarrow \infty} \frac{V_{out}}{V_{in}} = -10 \quad 20 \log_{10} 1 - 10 = 20$$


(ii) 20

**P14:** On the axes below, draw the Bode magnitude plot for this circuit. Label all important features of the plot.

13 P13 2 / 2

✓ - **0 pts** Correct (-\$\\$\\infty\$ at low frequencies and 20dB at high frequencies)

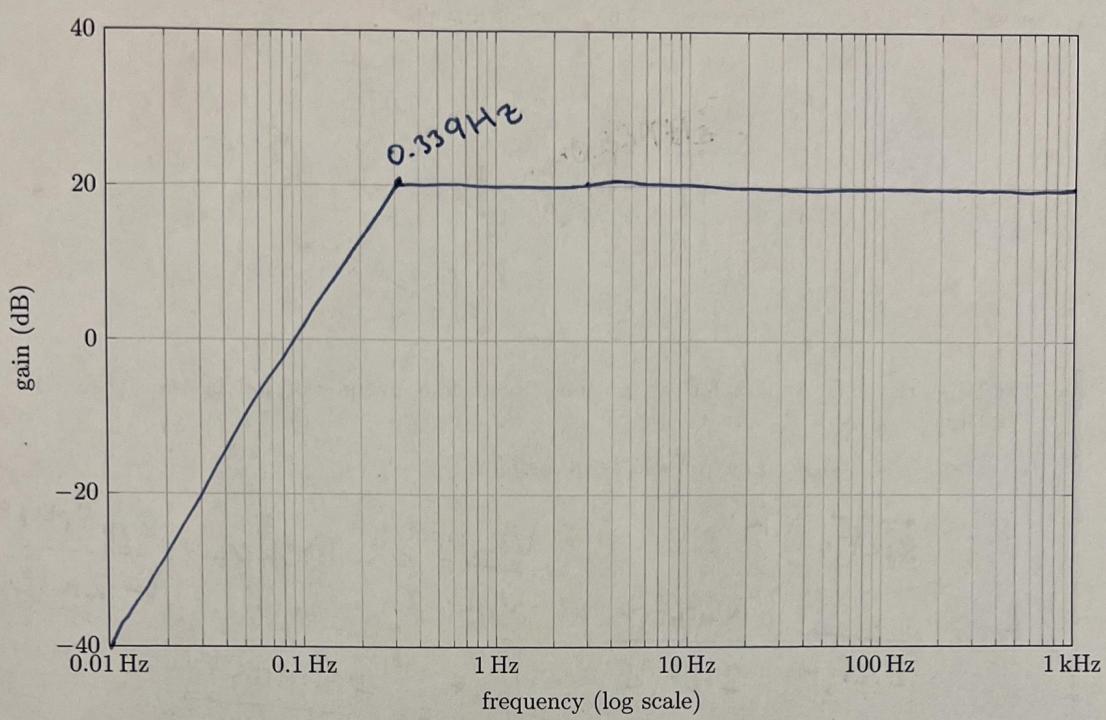- **0.1 pts** Said +infinity at low frequencies
- **0.1 pts** gave linear gain at low frequencies
- **0.5 pts** Forgot to convert to dB
- **0.5 pts** incorrect dB conversion
- **0.5 pts** incorrect at low frequencies
- **0.5 pts** incorrectly said approaches 0dB at high frequencies
- **0.5 pts** incorrect at high frequencies
- **0.5 pts** Incorrect work or derivation
- **1 pts** Incorrect
- **1.5 pts** Incorrect
- **0.2 pts** Small error
- **2 pts** no work
- **2 pts** Problem blank




P15: Using your Bode magnitude plot, is this a lowpass, highpass, bandpass or bandstop filter?

Highpass filter

14 P14 3 / 3

- ✓ - 0 pts Correct (corner frequency .3, high pass 20dB)
- 0.1 pts minor error
- 0.3 pts slope mislabeled
- 0.3 pts Corner frequency unlabeled
- 0.5 pts slope at low frequencies not specified or ambiguous
- 0.5 pts Ambiguous corner frequency
- 0.5 pts incorrect high frequency gain
- 0.5 pts slope at low frequencies should be 20dB/decade
- 1 pts Wrong corner frequency
- 1 pts line should be flat at high frequencies
- 1.5 pts Ambiguous/unlabeled graph with generally correct shape
- 2 pts drew lowpass filter
- 0 pts Carry over error from P12 or P13
- 3 pts no work
- 3 pts Problem blank / Major error
- 0.1 pts Wrong corner frequency on graph

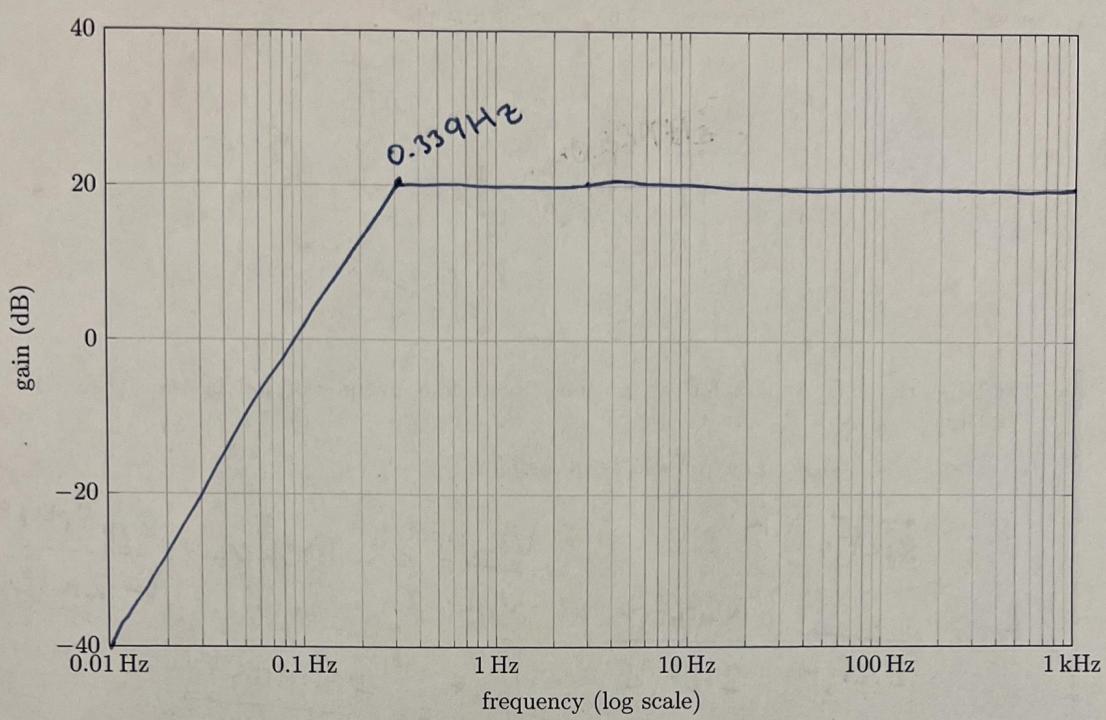

P15: Using your Bode magnitude plot, is this a lowpass, highpass, bandpass or bandstop filter?

Highpass filter


15 P15 1 / 1

✓ - **0 pts** Correct (high pass)

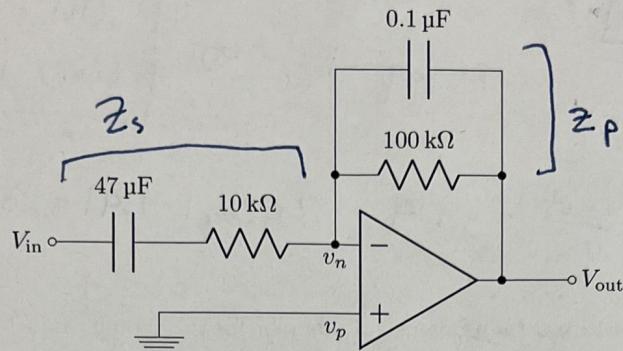- **0.5 pts** incorrect

- **1 pts** no work

Finally, here's the circuit we're going to build. For questions P16 through P20, consider this circuit.



- P16:** Use Kirchoff's current law, applied at the node at the inverting (-) input to the op-amp,  $v_n$ , to find a relationship between  $V_{in}$ ,  $V_{out}$  and  $v_n$ , in terms of  $Z_s$ , the combined impedance of the  $47 \mu F$  capacitor and the  $10 k\Omega$  resistor in series, and  $Z_p$ , the combined impedance of the  $0.1 \mu F$  capacitor and the  $100 k\Omega$  resistor in parallel. You can assume that the op-amp is ideal.

$$\frac{V_{in}}{Z_s} = -\frac{V_{out}}{Z_p}$$

$$\frac{V_{in}}{1+2\pi R f_{jc}} = -\frac{V_{out}}{100 k\Omega}$$

$$\frac{V_{out}}{V_{in}} = \frac{100 k\Omega}{1+2\pi Rms f_j} \cdot \frac{2\pi f_{jc}}{1+2\pi R f_{jc}}$$

$$V_{out} = -V_{in} \frac{9.4 \pi f_{jc}}{(1+2\pi Rms f_j)(1+0.94 \pi f_j)}$$

- P17:** Find an equation for the transfer function of this circuit by rearranging your equation from P16, and substituting in equations for  $Z_p$  and  $Z_s$  (in terms of  $f$ , resistances and capacitances).

Leave your answer in the form  $\frac{j f}{(1+j \frac{f}{f_{c1}})(1+j \frac{f}{f_{c2}})}$ .

$$f_{c1} = \frac{1}{9.4 \pi} = 0.0339 \text{ Hz}$$

$$f_{c2} = \frac{1}{20 \pi ms} = 15.915 \text{ Hz}$$

$$f_{c3} = \frac{1}{0.94 \pi} = 0.339 \text{ Hz}$$

$$\frac{V_{out}}{V_{in}} = -\frac{j \frac{f}{0.0339}}{(1+j \frac{f}{15.915})(1+j \frac{f}{0.339})}$$

- P18:** What is the magnitude of this transfer function, in dB, (i) at very low frequencies? (ii) at very high frequencies? (iii) between the two corner frequencies?


*Hint: There's a corner frequency associated with each of the terms in the denominator. Between the two corner frequencies,  $j f$  will dominate one of these terms, while the 1 will still dominate the*

16 P16 1 / 1

✓ - 0 pts Correct

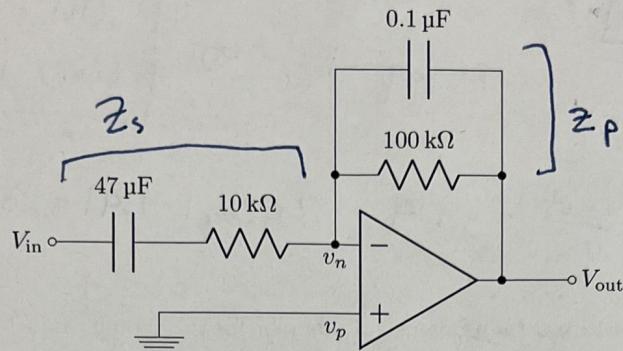- 0.1 pts sign error
- 0.2 pts Error(s) #1
- 0.25 pts One incorrect current equation
- 0.5 pts should be a nodal equation
- 0.5 pts answer not simplified
- 1 pts no work
- 1 pts Incorrect
- 1 pts problem blank
- 0.2 pts Nodal equation set up incorrectly

Finally, here's the circuit we're going to build. For questions P16 through P20, consider this circuit.



- P16:** Use Kirchoff's current law, applied at the node at the inverting (-) input to the op-amp,  $v_n$ , to find a relationship between  $V_{in}$ ,  $V_{out}$  and  $v_n$ , in terms of  $Z_s$ , the combined impedance of the  $47 \mu F$  capacitor and the  $10 k\Omega$  resistor in series, and  $Z_p$ , the combined impedance of the  $0.1 \mu F$  capacitor and the  $100 k\Omega$  resistor in parallel. You can assume that the op-amp is ideal.

$$\frac{V_{in}}{Z_s} = -\frac{V_{out}}{Z_p}$$

$$\frac{V_{in}}{1+2\pi R f_{jc}} = -\frac{V_{out}}{100 k\Omega}$$

$$\frac{V_{out}}{V_{in}} = \frac{100 k\Omega}{1+2\pi Rms f_j} \cdot \frac{2\pi f_{jc}}{1+2\pi R f_{jc}}$$

$$V_{out} = -V_{in} \frac{9.4 \pi f_{jc}}{(1+2\pi Rms f_j)(1+0.94 \pi f_j)}$$

- P17:** Find an equation for the transfer function of this circuit by rearranging your equation from P16, and substituting in equations for  $Z_p$  and  $Z_s$  (in terms of  $f$ , resistances and capacitances).

Leave your answer in the form  $\frac{j f}{(1+j \frac{f}{f_{c1}})(1+j \frac{f}{f_{c2}})}$ .

$$f_{c1} = \frac{1}{9.4 \pi} = 0.0339 \text{ Hz}$$

$$f_{c2} = \frac{1}{20 \pi ms} = 15.915 \text{ Hz}$$

$$f_{c3} = \frac{1}{0.94 \pi} = 0.339 \text{ Hz}$$

$$\frac{V_{out}}{V_{in}} = -\frac{j \frac{f}{0.0339}}{(1+j \frac{f}{15.915})(1+j \frac{f}{0.339})}$$

- P18:** What is the magnitude of this transfer function, in dB, (i) at very low frequencies? (ii) at very high frequencies? (iii) between the two corner frequencies?

*Hint: There's a corner frequency associated with each of the terms in the denominator. Between the two corner frequencies,  $j f$  will dominate one of these terms, while the 1 will still dominate the*

17 P17 3 / 3

✓ - 0 pts Correct

- 0 pts Carry over error
- 0.2 pts incorrect sign
- 0.2 pts missing j
- 0.5 pts algebra error

- 1.5 pts denominator should have higher order f terms

- 2 pts wrong approach

- 3 pts No submission

- 0.75 pts Right approach but no numerical values given/not simplified to std form

- 0.2 pts One incorrect fc

- 1.5 pts No work

- 0.3 pts Not in standard form

- 0.3 pts Answer not simplified

- 0.1 pts missing fc1

- 3 pts problem blank

other.

$$\lim_{f \rightarrow 0} \frac{V_{out}}{V_{in}} = 0$$

$$20 \log |1| = -\infty$$


$$\lim_{f \rightarrow \infty} \frac{V_{out}}{V_{in}} = 0$$

$$f = 15.9 \quad \frac{V_{out}}{V_{in}} = -4.9 \quad 20 \log |-4.9| = 13.796$$

$$f = 0.339$$

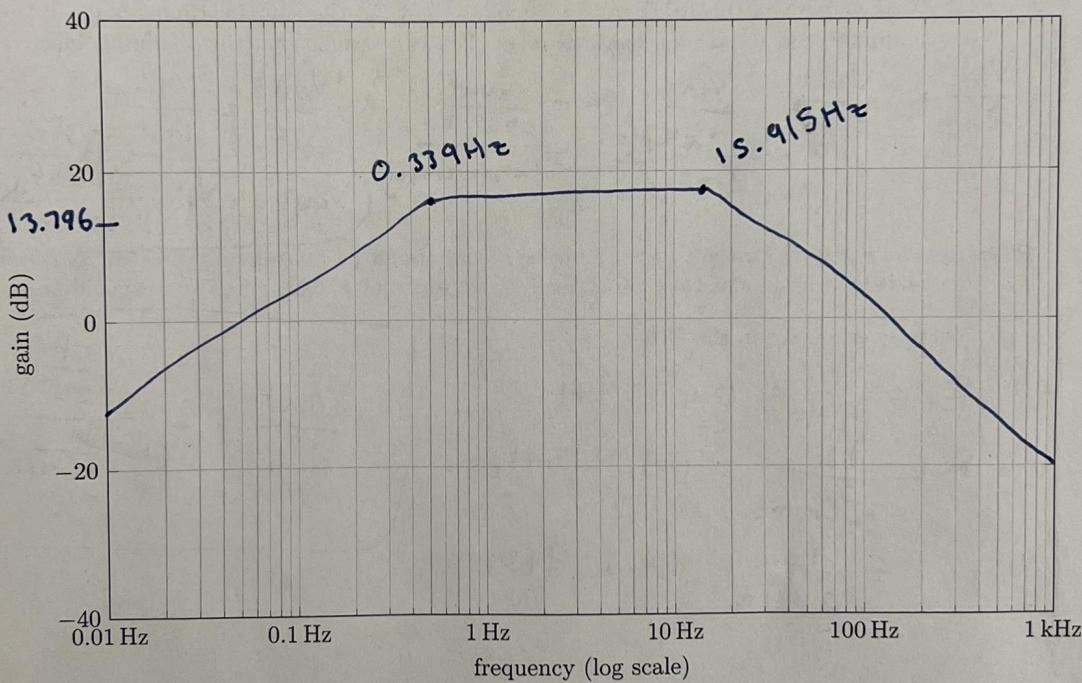- (i)  $-\infty$   
 (ii)  $-\infty$   
 (iii) 13.796

P19: On the axes below, draw the Bode magnitude plot for this circuit. Label all important features of the plot.



P20: Using your Bode magnitude plot, is this a lowpass, highpass, bandpass or bandstop filter?

Bandpass filter

18 P18 2 / 2

✓ - **0 pts** Correct (should approach  $-\infty$  for high and low frequencies, passband should have gain of 20dB)

- **0.5 pts** no answer for bandpass gain
- **0.5 pts** Incorrect bandpass gain (accept anything between 10-20dB)
- **0.5 pts** infinity instead of  $-\infty$
- **0.5 pts** Incorrectly said zero for low/high frequency
- **0.5 pts** incorrect low frequencies
- **0.5 pts** incorrect high frequencies
- **2 pts** no work
- **0.5 pts** Did not convert to dB
- **2 pts** problem blank
- **0.4 pts** No answer for high/low frequency case.
- **1 pts** no numerical value given for multiple regions

other.

$$\lim_{f \rightarrow 0} \frac{V_{out}}{V_{in}} = 0$$

$$20 \log |1| = -\infty$$


$$\lim_{f \rightarrow \infty} \frac{V_{out}}{V_{in}} = 0$$

$$f = 15.9 \quad \frac{V_{out}}{V_{in}} = -4.9 \quad 20 \log |-4.9| = 13.796$$

$$f = 0.339$$

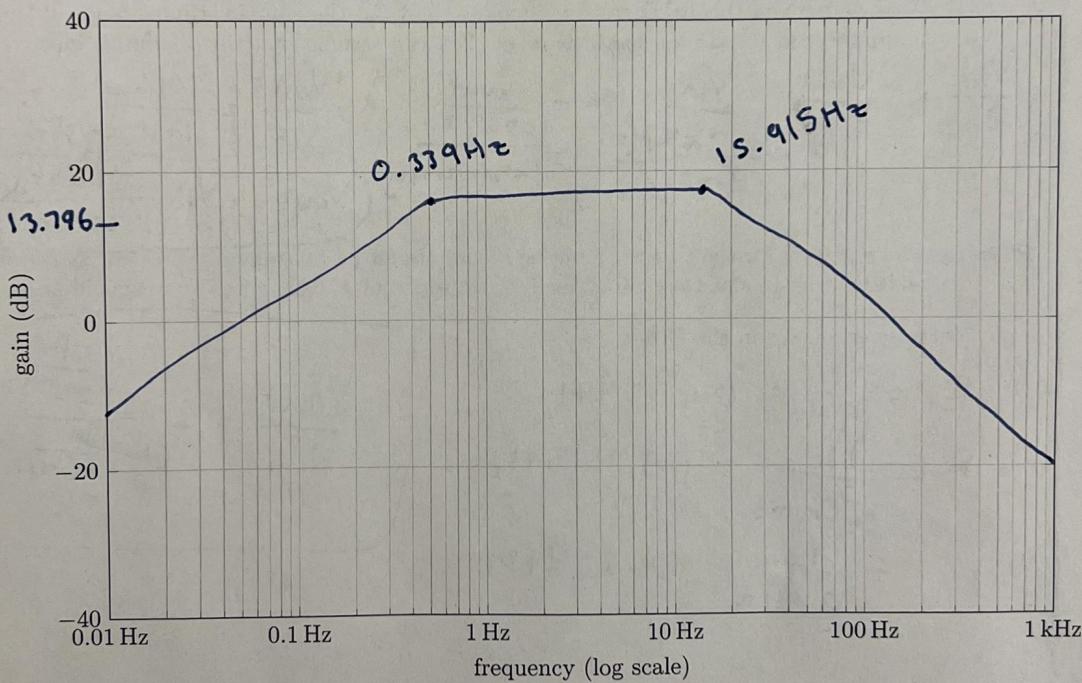- (i)  $-\infty$   
 (ii)  $-\infty$   
 (iii) 13.796

P19: On the axes below, draw the Bode magnitude plot for this circuit. Label all important features of the plot.



P20: Using your Bode magnitude plot, is this a lowpass, highpass, bandpass or bandstop filter?

Bandpass filter

19 P19 3 / 3

- ✓ - **0 pts** Correct (bandpass 20dB, corner frequencies at .33 and 15.9 Hz)
- **0.3 pts** said slope is +/- 1 for low and high frequency regions
- **0.3 pts** Low corner frequency incorrectly graphed
- **0.3 pts** High corner frequency incorrectly graphed
- **0.5 pts** one incorrect corner frequency
- **0.5 pts** graphing errors (see comments or graph)
- **0.5 pts** Incorrect bandpass gain
- **1 pts** Incorrect corner frequencies
- **0.5 pts** slope incorrect (should be 20db/decade)
- **0.5 pts** Corner frequencies not labeled
- **1 pts** forgot to label corner frequencies
- **2 pts** Not shaped like a bandpass filter
- **1 pts** Incorrect low/high frequency behavior
- **3 pts** Incomplete
- **0 pts** Carry over error from P18, but graph is correct.
- **1.5 pts** Graph vague, corner frequencies not labeled but correct shape

other.

$$\lim_{f \rightarrow 0} \frac{V_{out}}{V_{in}} = 0$$

$$20 \log |1| = -\infty$$


$$\lim_{f \rightarrow \infty} \frac{V_{out}}{V_{in}} = 0$$

$$f = 15.9 \quad \frac{V_{out}}{V_{in}} = -4.9 \quad 20 \log |-4.9| = 13.796$$

$$f = 0.339$$

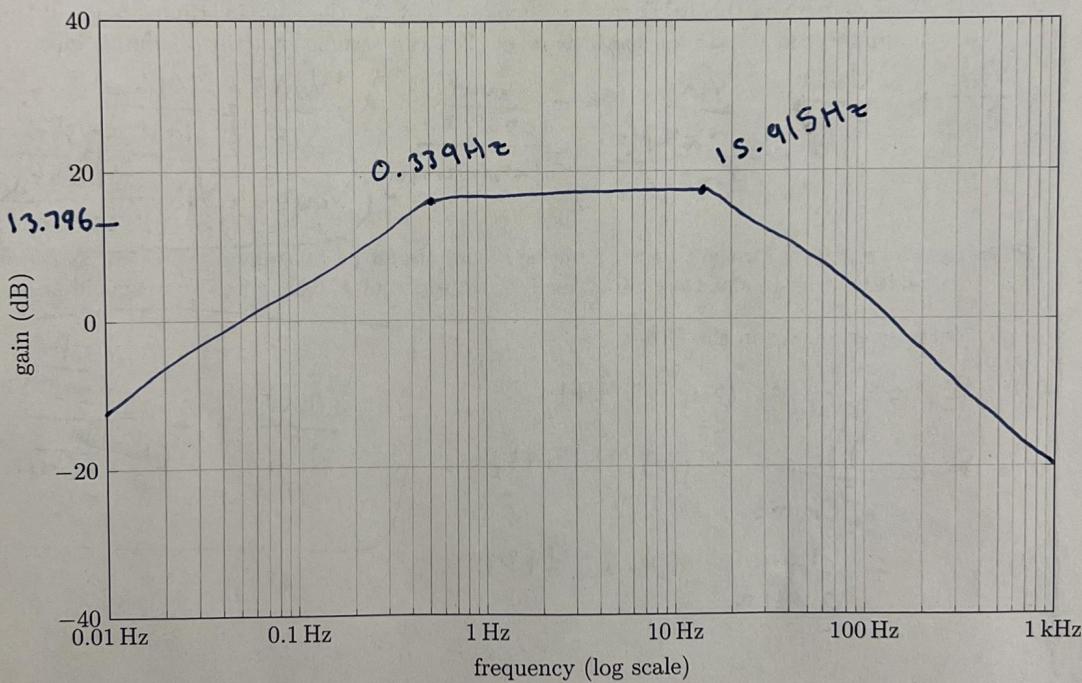- (i)  $-\infty$   
 (ii)  $-\infty$   
 (iii) 13.796

P19: On the axes below, draw the Bode magnitude plot for this circuit. Label all important features of the plot.



P20: Using your Bode magnitude plot, is this a lowpass, highpass, bandpass or bandstop filter?

Bandpass filter

20 P20 1/1

✓ - 0 pts Correct (Bandpass)

- 0.5 pts Incorrect

- 1 pts no submission